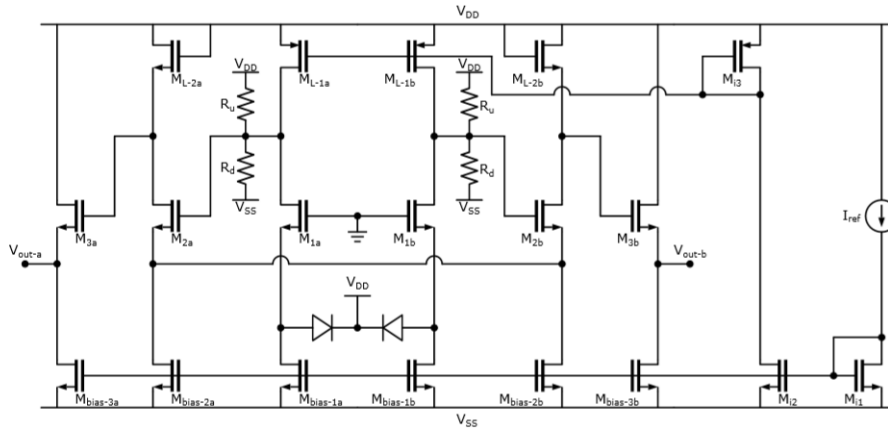


EE214A Design Project

Jay Smith


November 17, 2019



The amplifier under evaluation has 3 stages: Common Gate (CG), Common Source (CS), and Common Drain (CD). In order to analyze, the circuit is broken down into its 3 stages and key parameters are summarized.

Parameter	Spec
Transresistance gain	42.5k
power consumption	$\leq 2\text{mW}$
bandwidth	$\geq 75\text{MHz}$
Output load resistance	20k
Output load capacitance	250fF


Common Gate:

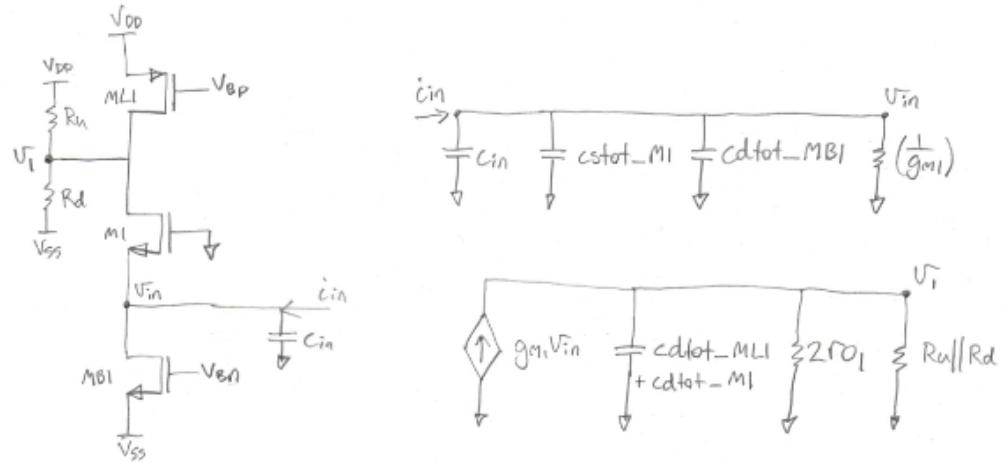

Low Frequency Characteristics		
Transimpedance Gain	$R_u \parallel R_d$	
R_{in}	$1/g_{m1}$	$V_{ov1}/(2 \cdot I_{D1})$
R_{out}	$2 \cdot r_{o1}$	$2/(\lambda \cdot I_{D1})$

Common Source:

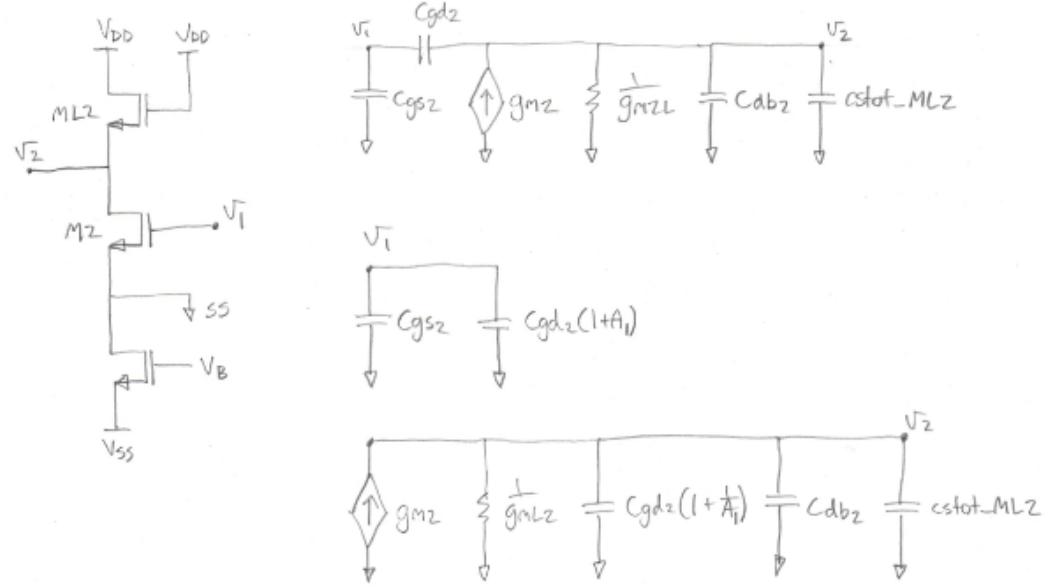The source of the common source stage is referenced to virtual, small-signal ground in the DM half circuit.



$$A_1 = \frac{gm_2}{gm_{L2}} \quad (1)$$


$$A_1 = \frac{\frac{W}{L}_2 * V_{ov2}}{\frac{W}{L}_{2L} * V_{ov2L}} \quad (2)$$

$$A_1 = \sqrt{\frac{\frac{W}{L}_2}{\frac{W}{L}_{2L}}} \quad (3)$$

$$A_1 = \frac{V_{ov2L}}{V_{ov2}} \quad (4)$$

Low Frequency Characteristics	
Av	-gm ₂ /gm _{L2}
Rin	inf
Rout	1/gm _{L2}

Common Drain:

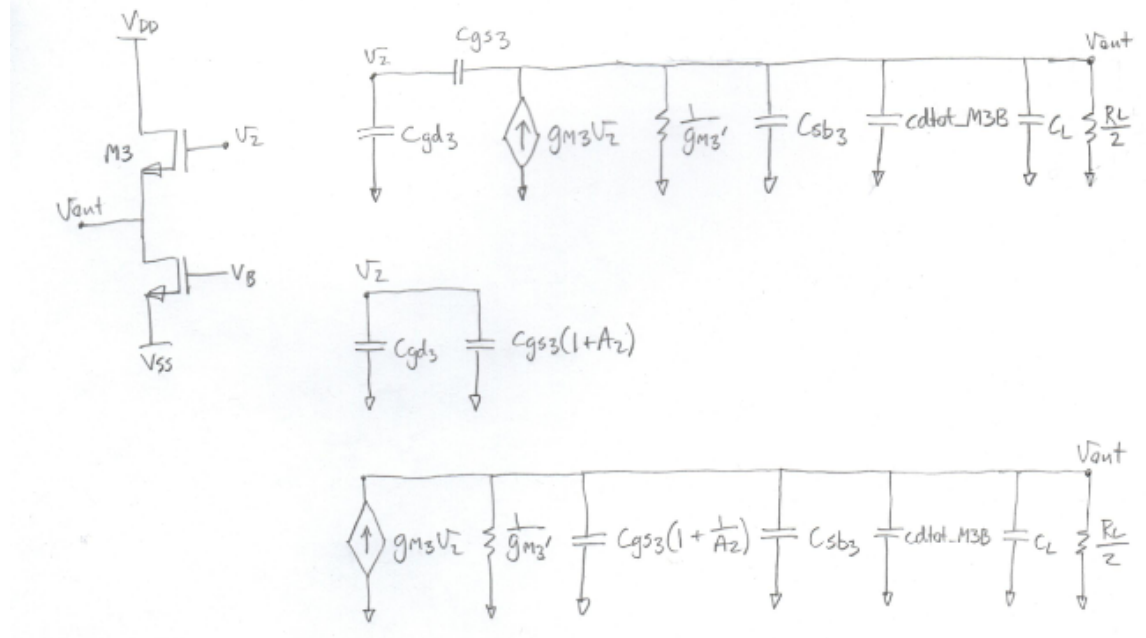

$$C_{LDM} = 500fF \quad (5)$$

$$R_{LDM} = 10k\Omega \quad (6)$$


Assuming $R_L/2$ much less than $1/g_{m3}$

$$A_2 = -g_{m3} * \frac{1}{g_{m3}'} || R_{LDM} \approx -0.84 \quad (7)$$

Low Frequency Characteristics	
A_v	approx. 0.84
R_{in}	inf
R_{out}	$1/g_{m3}'$

TIA amp:

Small-Signal Model

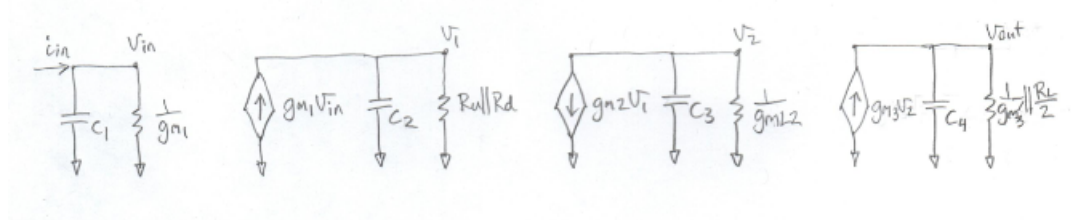

Low Frequency Transimpedance Gain:

$$\frac{v_{out}}{i_{in}} = (R_u || R_d) * \left(-\frac{gm_2}{gm_{L2}}\right) * 0.84 \quad (8)$$

BW

$$C_{LDM} = 500fF \quad (9)$$

$$R_{LDM} = 10k\Omega \quad (10)$$

$$C_1 = 100fF + c_{tot_M1} + c_{tot_MB1} \quad (11)$$

$$C_2 = c_{tot_ML1} + c_{tot_M1} + C_{gs2} + (1 + A_1) * C_{gd2} \quad (12)$$

$$C_3 = (1 + 1/A_1) * C_{gd2} + C_{db2} + c_{tot_ML2} + C_{gd3} + (1 + A_2) * C_{gs3} \quad (13)$$

$$C_4 = (1 + 1/A_2) * C_{gs3} + C_{sb3} + c_{tot_M3B} + 500fF \quad (14)$$

$$A_1 = \frac{gm_2}{gm_{L2}} \quad (15)$$

$$A_1 = \frac{\frac{W}{L}_2 * V_{ov2}}{\frac{W}{L}_{2L} * V_{ov2L}} \quad (16)$$

$$A_1 = \sqrt{\frac{\frac{W}{L}_2}{\frac{W}{L}_{2L}}} \quad (17)$$

$$A_1 = \frac{V_{ov2L}}{V_{ov2}} \quad (18)$$

$$A_2 = -g_{m3} * \frac{1}{g'_{m3}} || R_{LDM} \approx -0.84 \quad (19)$$

ZVTC bandwidth (conservative approximation)

$$b1 = \frac{1}{gm_1} * C_1 + (R_u || R_d) * C_2 + gm_{L2} * C_3 + (gm'_3 || R_L/2) * C_4 \quad (20)$$