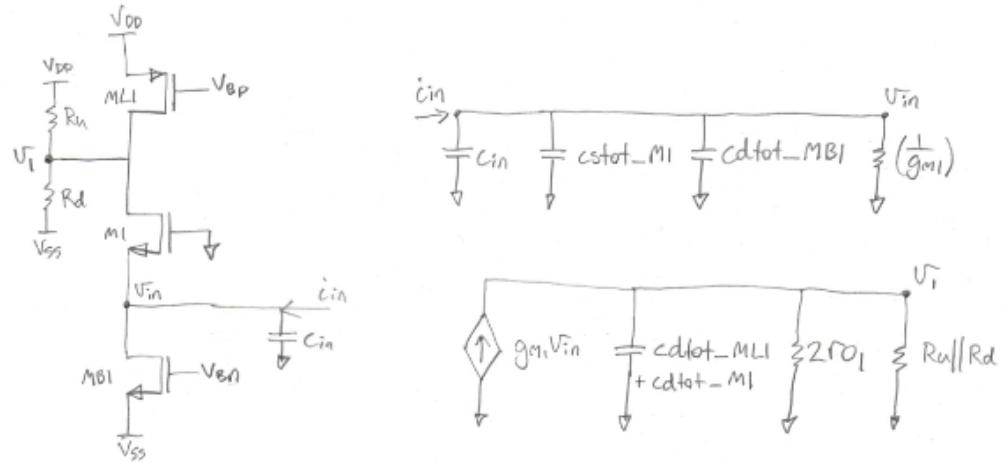





### Common Gate:



| Low Frequency Characteristics |                      |                            |
|-------------------------------|----------------------|----------------------------|
| Transimpedance Gain           | $R_u$ parallel $R_d$ |                            |
| $R_{in}$                      | $1/g_{m1}$           | $V_{ov1}/(2 \cdot I_{D1})$ |
| $R_{out}$                     | $2 \cdot r_{o1}$     | $2/(\lambda \cdot I_{D1})$ |
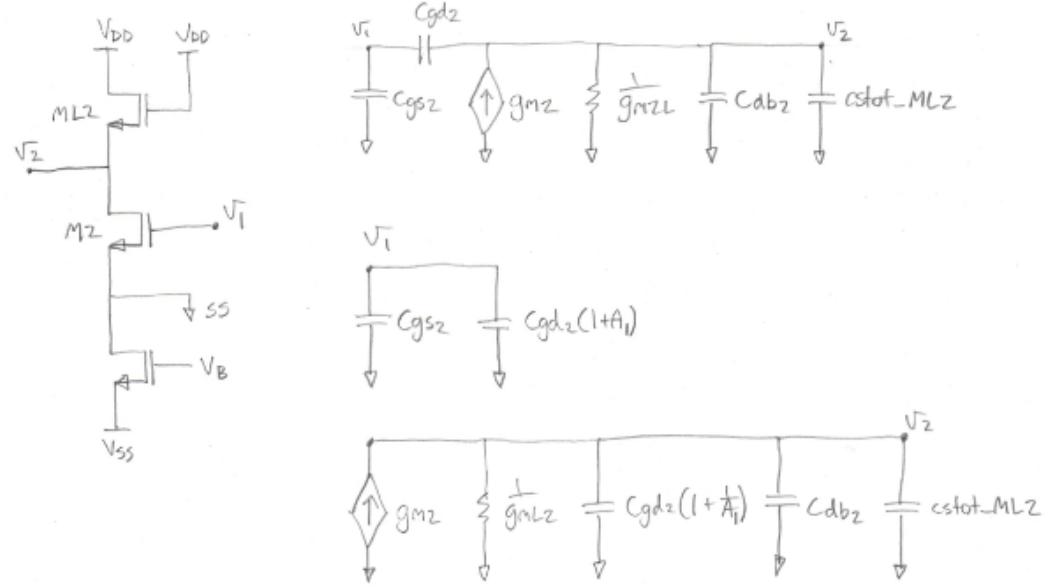
### Common Source:

The source of the common source stage is referenced to virtual, small-signal ground in the DM half circuit.



$$A_1 = \frac{gm_2}{gm_{L2}} \quad (1)$$


$$A_1 = \frac{\frac{W}{L}_2 * V_{ov2}}{\frac{W}{L}_{2L} * V_{ov2L}} \quad (2)$$

$$A_1 = \sqrt{\frac{\frac{W}{L}_2}{\frac{W}{L}_{2L}}} \quad (3)$$

$$A_1 = \frac{V_{ov2L}}{V_{ov2}} \quad (4)$$

| Low Frequency Characteristics |                                    |
|-------------------------------|------------------------------------|
| Av                            | -gm <sub>2</sub> /gm <sub>L2</sub> |
| Rin                           | inf                                |
| Rout                          | 1/gm <sub>L2</sub>                 |

### Common Drain:

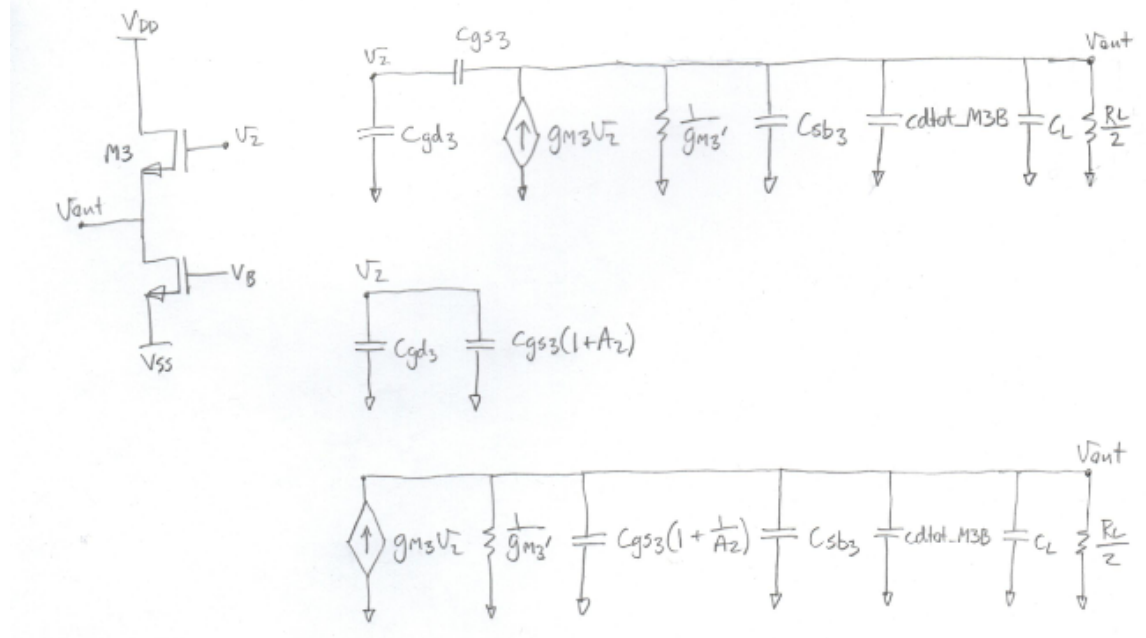

$$C_{LDM} = 500fF \quad (5)$$

$$R_{LDM} = 10k\Omega \quad (6)$$

Assuming  $R_L/2$  much less than  $1/g_{m3}$

$$A_2 = -g_{m3} * \frac{1}{g_{m3}'} || R_{LDM} \approx -0.84 \quad (7)$$

| Low Frequency Characteristics |              |
|-------------------------------|--------------|
| $A_v$                         | approx. 0.84 |
| $R_{in}$                      | inf          |
| $R_{out}$                     | $1/g_{m3}'$  |

## TIA amp:

Small-Signal Model

Low Frequency Transimpedance Gain:

$$\frac{v_{out}}{i_{in}} = (R_u || R_d) * (-\frac{gm_2}{gm_{L2}}) * 0.84 \quad (8)$$

BW

$$C_{LDM} = 500fF \quad (9)$$

$$R_{LDM} = 10k\Omega \quad (10)$$

$$C_1 = 100fF + cstot\_M1 + cdtot\_MB1 \quad (11)$$

$$C_2 = cdtot\_ML1 + cdtot\_M1 + C_{gs2} + (1 + A_1) * C_{gd2} \quad (12)$$

$$C_3 = (1+1/A_1)*C_{gd2}+C_{db2}+cstot\_ML2+C_{gd3}+(1+A_2)*C_{gs3} \quad (13)$$

$$C_4 = (1 + 1/A_2) * C_{gs3} + C_{sb3} + cdtot\_M3B + 500fF \quad (14)$$

$$A_1 = \frac{gm_2}{gm_{L2}} \quad (15)$$

$$A_1 = \frac{\frac{W}{L}_2 * V_{ov2}}{\frac{W}{L}_{2L} * V_{ov2L}} \quad (16)$$

$$A_1 = \sqrt{\frac{\frac{W}{L}_2}{\frac{W}{L}_{2L}}} \quad (17)$$

$$A_1 = \frac{V_{ov2L}}{V_{ov2}} \quad (18)$$

$$A_2 = -g_{m3} * \frac{1}{g'_{m3}} || R_{LDM} \approx -0.84 \quad (19)$$

ZVTC bandwidth (conservative approximation)

$$b1 = \frac{1}{g_{m1}} * C_1 + (R_u || R_d) * C_2 + gm_{L2} * C_3 + (gm'_3 || R_L/2) * C_4 \quad (20)$$