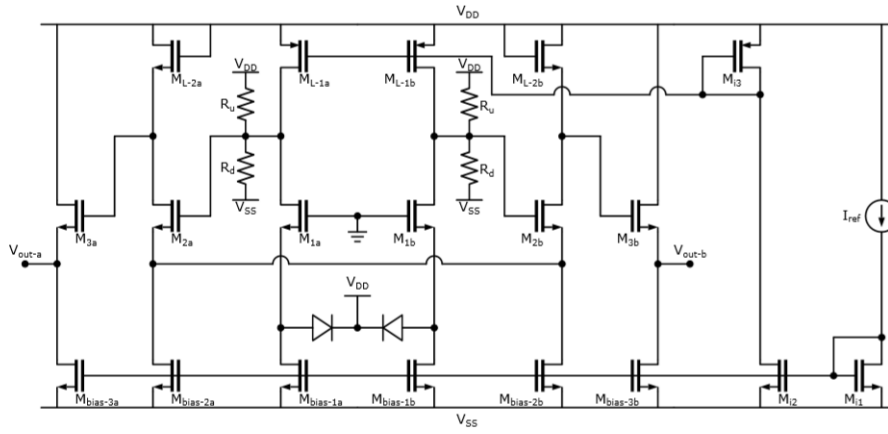


EE214A Design Project

Jay Smith


November 13, 2019



The amplifier under evaluation has 3 stages: Common Gate (CG), Common Source (CS), and Common Drain (CD). In order to analyze, the circuit is broken down into its 3 stages and key parameters are summarized.

Parameter	Spec
Transresistance gain	42.5k
Output load resistance	20k
Output load capacitance	250fF


Common Gate:

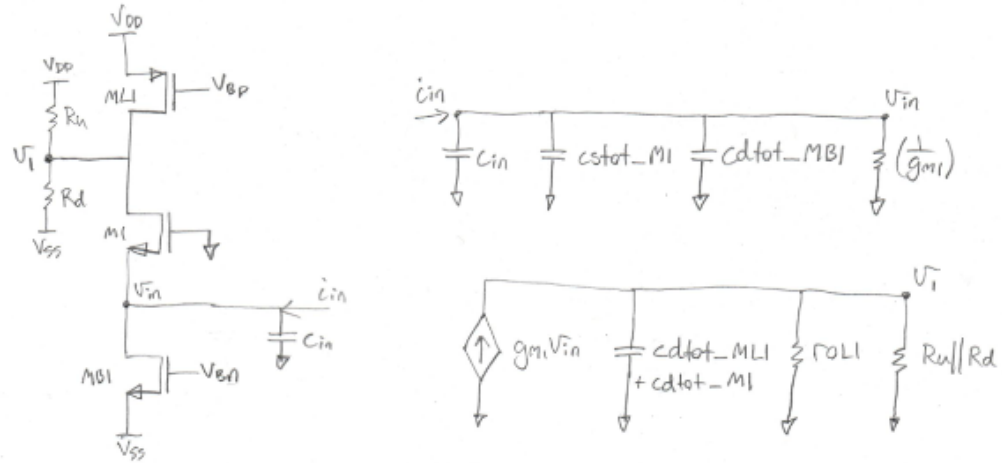

Low Frequency Characteristics	
Transimpedance Gain	R_u parallel R_d
R_{in}	$1/g_{m1}$
R_{out}	high

Common Source:

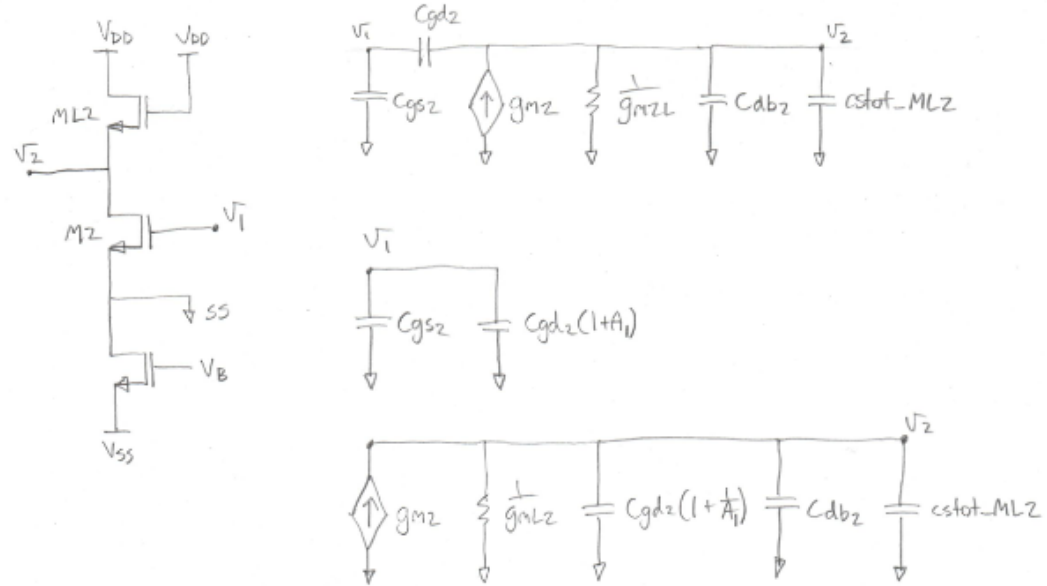The source of the common source stage is referenced to virtual, small-signal ground in the DM half circuit.




Where:

$$A_1 = \frac{gm_2}{gm_{L2}} \quad (1)$$

Low Frequency Characteristics	
Av	$-gm_2 \cdot R_{L2}$
Rin	inf
Rout	$1/gm_{L2}$

Common Drain:

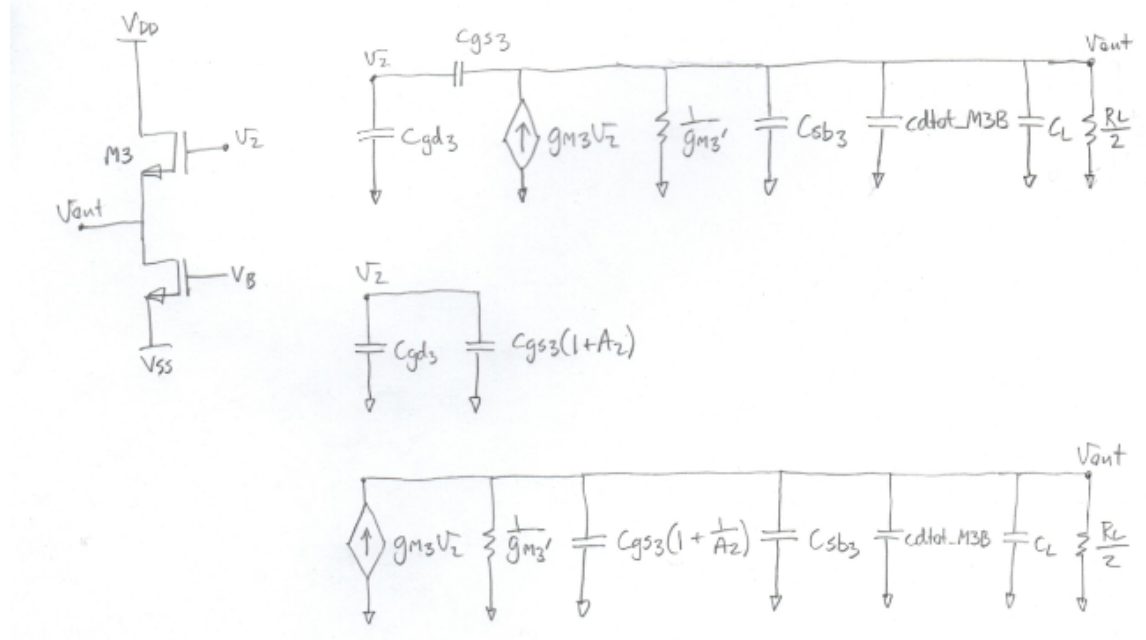

Where:

$$C_L = 250 \text{ fF} \quad (2)$$

$$R_L = 20 \text{ k}\Omega \quad (3)$$

Assuming $R_L/2$ much less than $1/g_{m3}$


$$A_2 \approx -\frac{g_{m3}}{g'_{m3}} \approx -0.84 \quad (4)$$

Low Frequency Characteristics	
A_v	approx. 0.84
R_{in}	inf
R_{out}	$1/g_{m3}'$

Low Frequency Transimpedance Gain:

$$\frac{v_{out}}{i_{in}} = (R_u || R_d) * \left(-\frac{gm_2}{gm_{L2}}\right) * 0.84 \quad (5)$$

TIA Amp Small-Signal Model

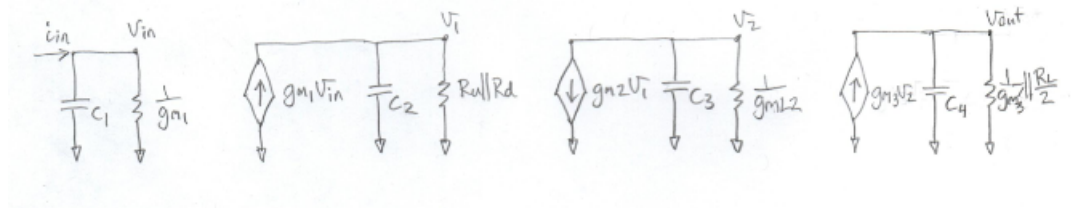

ZVTC bandwidth (conservative approximation)

$$b1 = \frac{1}{gm1} * C_1 + (R_u || R_d) * C_2 + gm_{L2} * C_3 + (gm'_3 || R_L/2) * C_4 \quad (6)$$

where

$$C_1 = 100fF + cstot_M1 + cdtot_MB1 \quad (7)$$

$$C_2 = cdtot_ML1 + cdtot_M1 + C_{gs2} + (1 + A_1) * C_{gd2} \quad (8)$$

$$C_3 = (1 + 1/A_1) * C_{gd2} + C_{db2} + cstot_ML2 + C_{gd3} + (1 + A_2) * C_{gs3} \quad (9)$$

$$C_4 = (1 + 1/A_2) * C_{gs3} + C_{sb3} + cdtot_M3B + 500fF \quad (10)$$

Where:

$$A_1 = \frac{gm_2}{gm_{L2}} \quad (11)$$

$$A_2 \approx -\frac{gm_3}{g'_{m3}} \approx -0.84 \quad (12)$$