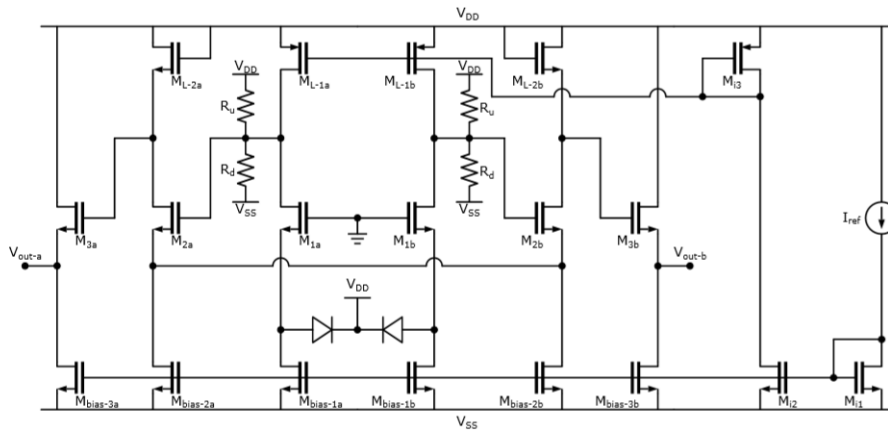


## EE214A Design Project

Jay Smith


November 14, 2019



The amplifier under evaluation has 3 stages: Common Gate (CG), Common Source (CS), and Common Drain (CD). In order to analyze, the circuit is broken down into its 3 stages and key parameters are summarized.

| Parameter               | Spec                |
|-------------------------|---------------------|
| Transresistance gain    | 42.5k               |
| power consumption       | $\leq 2\text{mW}$   |
| bandwidth               | $\geq 75\text{MHz}$ |
| Output load resistance  | 20k                 |
| Output load capacitance | 250fF               |


### Common Gate:

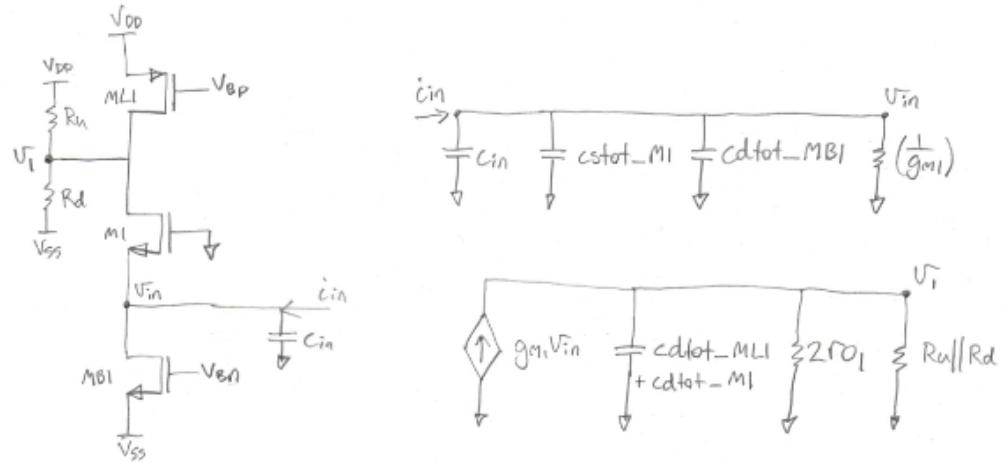

| Low Frequency Characteristics |                      |                            |
|-------------------------------|----------------------|----------------------------|
| Transimpedance Gain           | $R_u$ parallel $R_d$ |                            |
| $R_{in}$                      | $1/g_{m1}$           | $V_{ov1}/(2 \cdot I_{D1})$ |
| $R_{out}$                     | $2 \cdot r_{o1}$     | $2/(\lambda \cdot I_{D1})$ |
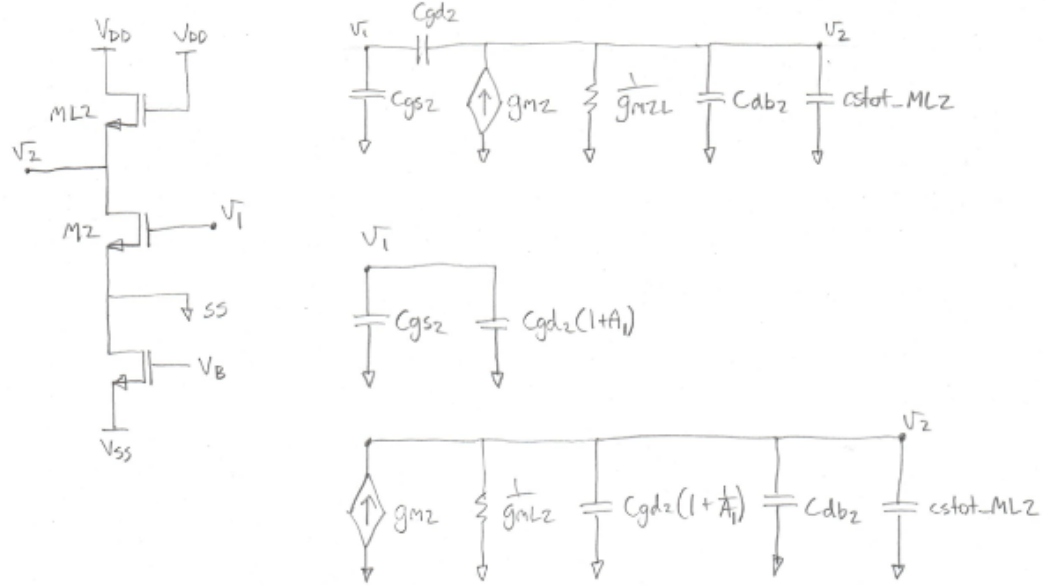
### Common Source:

The source of the common source stage is referenced to virtual, small-signal ground in the DM half circuit.




$$A_1 = \frac{gm_2}{gm_{L2}} \quad (1)$$

$$A_1 = \frac{\frac{W}{L}_2 * V_{ov2}}{\frac{W}{L}_{2L} * V_{ov2L}} \quad (2)$$

$$A_1 = \frac{\frac{W}{L}_2}{\frac{W}{L}_{2L}} * \frac{2}{V_{ov2L} * \left(\frac{gm}{I_D}\right)_2} \quad (3)$$

| Low Frequency Characteristics |                                    |
|-------------------------------|------------------------------------|
| Av                            | -gm <sub>2</sub> /gm <sub>L2</sub> |
| Rin                           | inf                                |
| Rout                          | 1/gm <sub>L2</sub>                 |

### Common Drain:

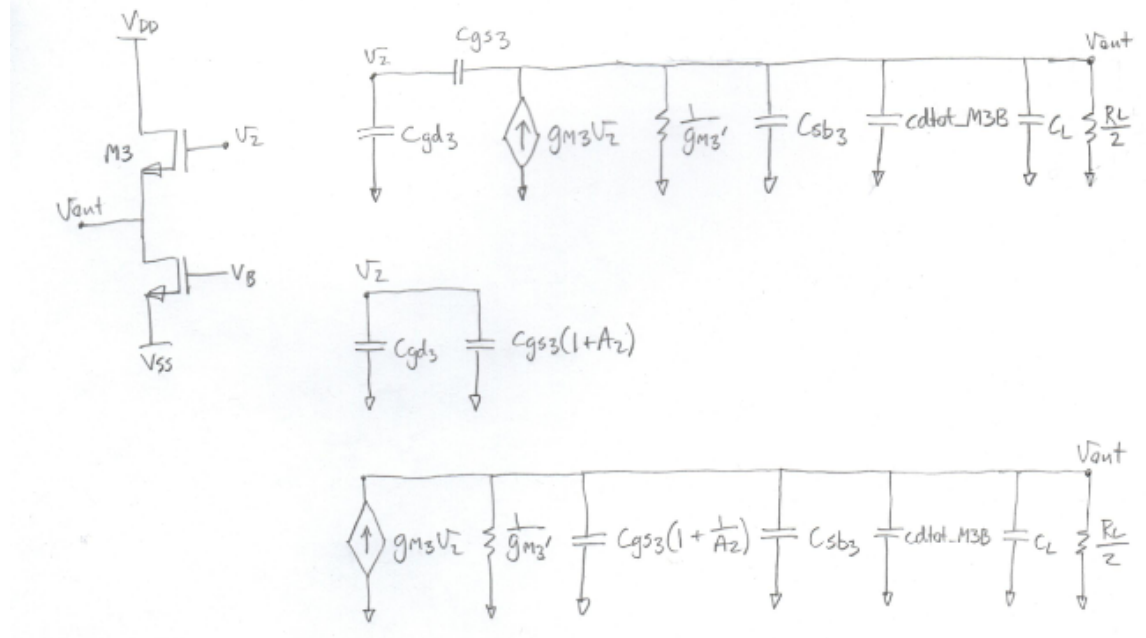

$$C_{LDM} = 500fF \quad (4)$$

$$R_{LDM} = 10k\Omega \quad (5)$$


Assuming  $R_L/2$  much less than  $1/g_{m3}$

$$A_2 \approx -\frac{g_{m3}}{g_{m3}'} \approx -0.84 \quad (6)$$

| Low Frequency Characteristics |              |
|-------------------------------|--------------|
| $A_v$                         | approx. 0.84 |
| $R_{in}$                      | inf          |
| $R_{out}$                     | $1/g_{m3}'$  |

## TIA amp:

### Small-Signal Model

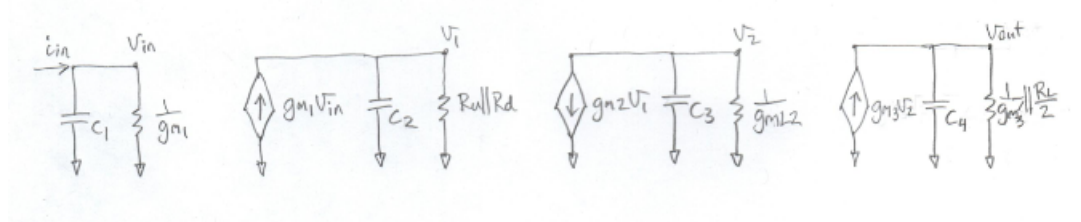

Low Frequency Transimpedance Gain:

$$\frac{v_{out}}{i_{in}} = (R_u || R_d) * \left(-\frac{gm_2}{gm_{L2}}\right) * 0.84 \quad (7)$$

BW

$$C_1 = 100fF + cstot\_M1 + cdtot\_MB1 \quad (8)$$

$$C_2 = cdtot\_ML1 + cdtot\_M1 + C_{gs2} + (1 + A_1) * C_{gd2} \quad (9)$$

$$C_3 = (1 + 1/A_1) * C_{gd2} + C_{db2} + cstot\_ML2 + C_{gd3} + (1 + A_2) * C_{gs3} \quad (10)$$

$$C_4 = (1 + 1/A_2) * C_{gs3} + C_{sb3} + cdtot\_M3B + 500fF \quad (11)$$

$$A_1 = \frac{gm_2}{gm_{L2}} \quad (12)$$

$$A_2 \approx -\frac{gm_3}{g'_{m3}} \approx -0.84 \quad (13)$$

ZVTC bandwidth (conservative approximation)

$$b1 = \frac{1}{gm_1} * C_1 + (R_u || R_d) * C_2 + gm_{L2} * C_3 + (gm'_3 || R_L/2) * C_4 \quad (14)$$